

# OPERATIONAL AMPLIFIER (OPAMP)


Page No. 8

(ANSWER SHEET)

The operational amplifier (OPAMP) is a direct-coupled amplifier with very high voltage gain, very high input impedance and very low output impedance. It can be applied to perform a wide variety of linear and non-linear operations by changing a few external circuit elements. This type of amplifier is usable in the frequency range from 0 to few MHz.

Originally OPAM was designed to perform some mathematical operations such as summation, subtraction, multiplication, differentiation, integration etc in analog computer. However, at the present days, a large variety of OPAMP are available almost all in IC forms and sold at a relatively low cost. Thereby, OPAMP has become very popular in electronic industry.

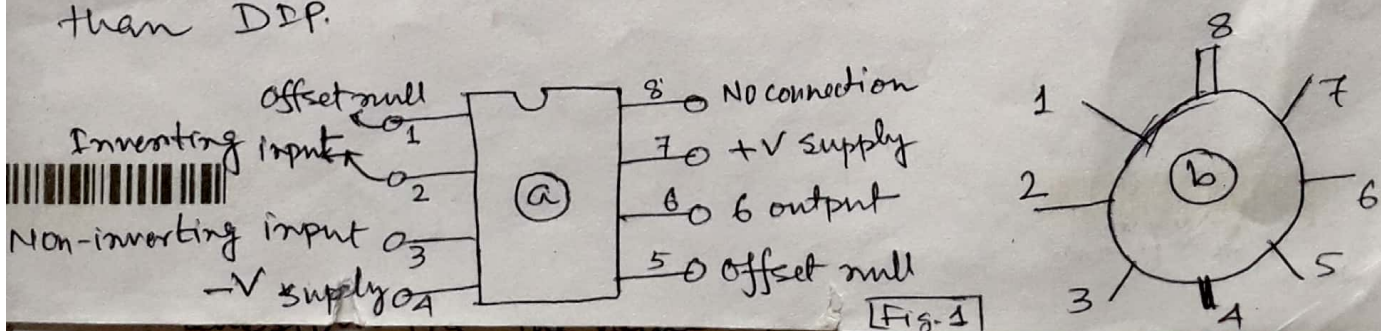OP-AMP is available in different packages such as 8-lead dual-in-line package (DIP) with two parallel lines of pins. The OP-AMP can also be fabricated in the form of TO-5 metal case with a circular array of wire leads or the flat-pack. The metal case has the advantage of somewhat higher power dissipation but it is costlier than DIP.





The pin configuration of the IC of widely used DIP-OPMP and ~~metal~~ metal case packages are shown in figure 1(a) and b respectively.

The ~~pos~~ positive (+V) and negative (-V) supply voltages are connected at the pins 7 and 4 respectively. No connection ~~req~~ required at the connection 8. The input is given in the terminals 2 or 3. If the input is given to the terminal 2, then the output will change its phase by  $180^\circ$  i.e. the output signal is inverted. That's why this input terminal is called inverting input terminal. However, if the input is given to the input terminal 3, then the output signal will be in the same phase of input signal. So this terminal is called non-inverting terminal. The output is measured across the pin 6. Terminals 1 and 5 are used for offset nulling, i.e. to make the output zero, when the input signal is zero.

The standard circuit symbol of an OP-AMP is shown in figure 2.

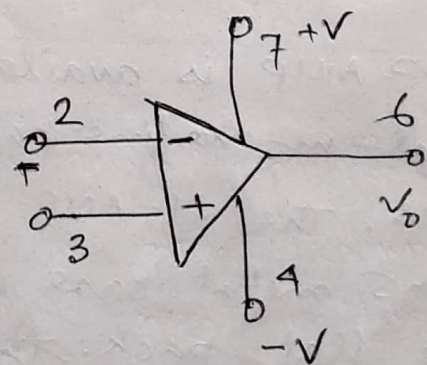


Fig-2



# Characteristics of an ideal OPAMP:

~~Fig. 10.3~~

~~Answer~~

The characteristics of an ideal OP-AMP are given below:

- (i) The open loop voltage gain of an ideal OPAMP is infinity ( $A = \infty$ ).
- (ii) The input impedance is infinite, whereas the output impedance is zero.
- (iii) Band gap of an ideal OP-AMP is infinite.
- (iv) An ideal OP-AMP is perfectly balanced i.e. when the input voltage is zero, then the output voltage will also be zero.
- (v) The characteristics of an ideal OP-AMP do not change with temperature i.e. it is linear.
- (vi) Common mode rejection ratio is infinite.
- (vii) Slew rate is infinite so that the output voltage changes simultaneously with input voltage-changes.

However, a practical OPAMP deviates from these ideal characteristics. For example, the open loop gain is not infinite, rather it  $\approx 2 \times 10^5$ , input impedance  $\approx 2 \text{ M}\Omega$ , output impedance  $\approx 75 \Omega$ , input offset voltage  $\sim 1 \text{ mV}$ .







The a.c. equivalent circuit of an OP-AMP is shown in figure 3. For an ideal OP-AMP, the input resistance  $R_i$  is infinite and the output impedance  $R_o$  is zero. For the practical OP-AMP, the output voltage ( $V_o$ ) is equal to the amplifier voltage gain  $A$  multiplied by the difference voltage ( $V_d = V_1 - V_2$ ).

$$\text{i.e. } V_o = A(V_1 - V_2).$$

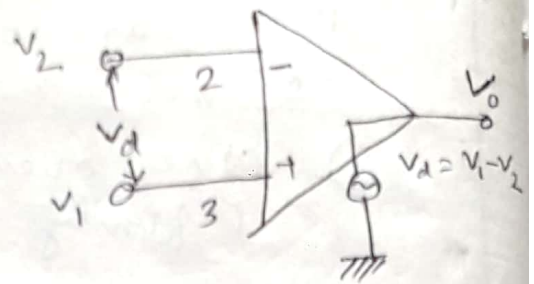which is measured through the ~~terminal~~ resistance  $R_o$ .



(a)

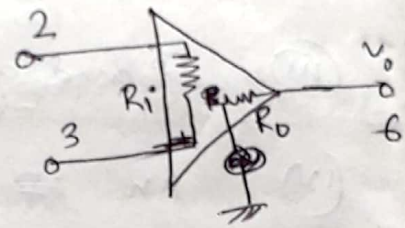

(b)

Fig-3

### Common mode rejection ratio (CMRR):

The OP-AMP is basically an amplifier which amplifies the difference in the input terminals. Therefore, if  $V_1$  and  $V_2$  are the input voltages given to the non-inverting and inverting terminals respectively, then the output voltage  $V_o$  of an ideal OPAMP is given by,

$$V_o = A_d(V_1 - V_2) \longrightarrow \text{①}$$

where  $A_d$  is the gain for the difference voltage  
 $V_d = V_1 - V_2$



Thus, if  $V_1 = V_2$ , then the output voltage  $V_o$  should be zero. But  this does not happen in reality, because the output of an op-AMP does not depend only on the difference voltage ( $V_d$ ) but also on the average voltage  $V_c = \frac{V_1 + V_2}{2}$ , called the common mode signal. This happens so due to lack in perfect ckt. symmetry.

Therefore,  $V_o = A_d V_d + A_c V_c$  ———— (2)

where,  $A_c$  is the voltage gain for common mode signal.

In ideal case, we expect  $A_d = \infty$  and  $A_c = 0$ . But in practice this is not true.

To express how successful the differential amplifier is in providing gain, one has to introduce a factor, called the common mode rejection ratio (CMRR) and defined as,

$$CMRR = \left| \frac{A_d}{A_c} \right| \text{ ———— (3)}$$

This CMRR actually considers as the figure of merit of a differential amplifier. Higher the value of CMRR, better is the performance.

For large values of CMRR, it often expresses in dB as,

$$CMRR (dB) = 20 \log_{10} \left| \frac{A_d}{A_c} \right| \text{ ———— (4)}$$

DC OPAMP 741 has a CMRR of about 90dB.



## OP AMP offset voltage and current

An ideal OPMP is perfectly balanced i.e. the output  $V_o = 0$  when the two inputs are equal ( $V_1 = V_2$ ). In practical OP-AMP an unbalance is caused due to mismatch of input transistors. This mismatch causes the flow of unequal <sup>bias</sup> currents through the input terminals, which results in a non-zero output voltage, without any input voltage. This ~~of~~ output voltage is called offset voltage and can be balanced by applying a small d.c. voltage ( $\sim \text{mV}$ ) between the input terminals.

The voltage which should be applied bet<sup>n</sup> the input terminals to balance the amplifier is called input offset voltage. The voltage that appears at the output terminal with the two ~~to~~ input terminals grounded is called the output offset voltage.

\* The input offset voltage is usually very small ( $\sim \text{mV}$ ) and hence can be neglected in many applications with relatively large input voltages. But there are some certain cases where its effect can not be neglected.

\*\* The input offset current is defined as the difference between the two bias currents entering into the input terminals of balanced amplifiers. Further, the input bias current is defined as the average of two separate currents entering



## Concept of Virtual ground

Figure 4 shows the basic diagram of an inverting OPAMP which employs -ve feedback through the resistor  $R_2$ .

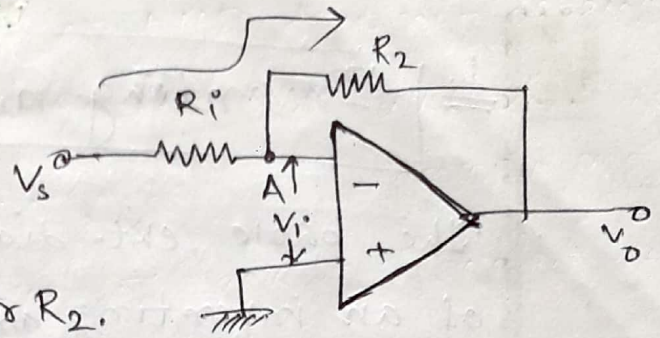


Fig. 4

The -ve feedback voltage tries to cancel the input voltage at A and tries to keep the voltage ~~at A~~ at A to ground potential.

Let, the potential at A is  $V_i$ , then the output voltage  $V_o = -AV_i$ . Since the open loop gain (A) is infinite, for a ~~non~~ finite  $V_o$  we must have  $V_i \rightarrow 0$ . Furthermore, since the input impedance  $R_i \rightarrow \infty$ , practically no current passes through the OPAMP. This point A is called a virtual ground.

The word virtual is used to imply that ~~though the~~ though the point A is not directly connected to the ground, but it behaves like a ground point. However, it is not the actual ground.



# APPLICATIONS OF OPAMP

## 1. Inverting amplifier

The basic ckt. diagram of an inverting amplifier using an OPAMP is shown in fig 5. Here,

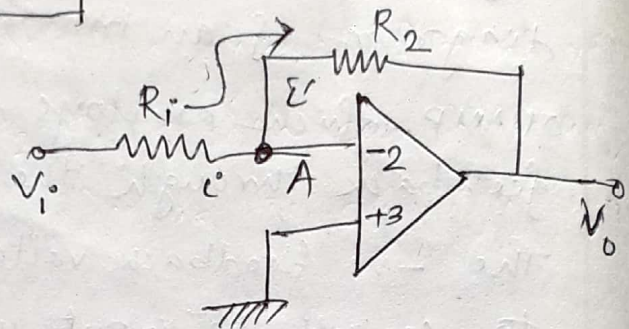


fig 5

the input voltage ( $V_i$ ) is applied to the inverting ~~and~~ input terminal through the resistor  $R_i$ . The non-inverting terminal is grounded. Since the input impedance of an ideal OPAMP is infinite, hence the point A will behave as virtual ground. The point A is connected to the output through the feedback resistance  $R_2$ . The output voltage is  $V_o$ .

Since, the input impedance is infinite, current will flow through A to the output via  $R_2$ . Let the current entering at A is  $i$  and that leaving A is  $i'$ . Then according to KCL,

$$i = i'$$

$$\text{Now, } i = \frac{V_i - V_x}{R_i}$$

$$\text{also, } i' = \frac{V_x - V_o}{R_2}$$

$$\boxed{V_x = \text{potential at A} \\ \text{which is essentially} \\ = 0}$$

$$\therefore \frac{V_i - V_x}{R_i} = \frac{V_x - V_o}{R_2} \Rightarrow \frac{-V_o}{R_2} = \frac{V_i}{R_i} \quad [V_x = 0]$$

$$\Rightarrow \boxed{V_o = -\frac{R_2}{R_i} V_i} \rightarrow \textcircled{5}$$



So the closed loop gain is  $= \frac{V_o}{V_i} = -\frac{R_2}{R_1}$ .

The negative sign indicates that the output is  $180^\circ$  out of phase with the input i.e. the output voltage is in opposite phase of the input voltage, which means this amplifier inverts the input voltage. Thus, it is called an inverting amplifier.

The gain depends only on the ratio of  $R_2$  and  $R_1$  and therefore independent of OPAMP parameters.

## 2. Scale changer

For an inverting amplifier using OPAMP, the output voltage is obtained as,

$$V_o = -\frac{R_2}{R_1} V_i = -K V_i$$

where,  $K = \frac{R_2}{R_1}$  is an accurately known constant.

Thus, the ckt multiplies the input voltage by  $-K$ , called the scale factor. Therefore the output voltage scale is obtained by multiplying the input voltage scale by  $-K$ . Thus, the inverting amplifier can act as a scale changer.

## ③ Phase shifter

Let, the resistances  $R_1$  and  $R_2$  of an inverting amplifier are replaced by the impedances  $Z_1$  and  $Z_2$ , then,

$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1}$$

If,  $Z_1$  and  $Z_2$  are so chosen that they have same amplitude but different phases, then



$$\frac{V_o}{V_i} = -\frac{Z_2 e^{j\phi_2}}{Z_1 e^{j\phi_1}} \quad \text{where } \phi_1 \text{ and } \phi_2 \text{ are angles of } Z_1 \text{ and } Z_2.$$

(ANSWER SHEET)

$$\therefore \frac{V_o}{V_i} = e^{j(\pi + \phi_2 - \phi_1)}$$

Therefore, OPAMP can shift the phase of input voltage  $V_i$  by the angle  $(\pi + \phi_2 - \phi_1)$ , which can have any value between 0 to  $360^\circ$ , whereas the amplitudes remain constant.

## NON-INVERTING AMPLIFIER

The basic ckt. diagram of a non-inverting amplifier using OPAMP is shown in Fig. 6. Here

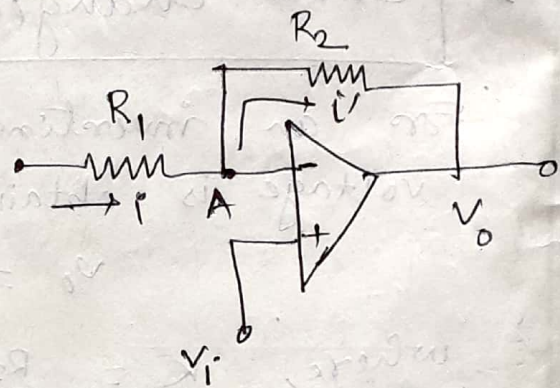


Fig. 6

the input voltage is applied to the non-inverting terminal. The inverting input terminal is ~~for~~ grounded through a resistance  $R_1$ .

Since, the input impedance of the OPAMP is infinite, no current will pass through the OPAMP. Therefore, the potential at the point A is equal to  $V_i$ .

Let,  $i$  and  $i'$  current flow through  $R_1$  and  $R_2$  respectively. Then applying KCL at A, we have,  $i = i'$

$$\text{Now, } i = \frac{-V_i + 0}{R_1} = -\frac{V_i}{R_1} \quad \text{and, } i' = \frac{V_i - V_o}{R_2}$$



$$\frac{V_i - V_o}{R_2} = -\frac{V_i}{R_1} \Rightarrow \frac{V_o}{R_2} = V_i \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\Rightarrow V_o = R_2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right) V_i$$

$$\Rightarrow \boxed{V_o = \left( 1 + \frac{R_2}{R_1} \right) V_i}$$

The gain of the amplifier (A) =  $\left( 1 + \frac{R_2}{R_1} \right)$ .

The output voltage  $V_o$  is in the same phase as that of  $V_i$  i.e. the phase of the output does not change. Hence, the amplifier is called non-inverting amplifier.

### Unity gain follower:

We have the gain of a non-inverting amplifier using OPAMP is

$$A_{\text{no}} = \left( 1 + \frac{R_f}{R_i} \right)$$

It is clear from this equation that the loop gain becomes unity when  $\frac{R_f}{R_i} = 0$  that means either  $R_f = 0$  or  $R_i = \infty$ . The amplifier is then called a unity gain buffer or unity gain follower.

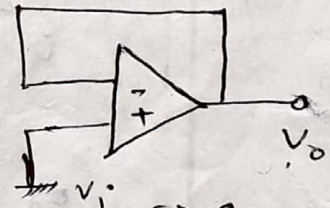


Fig-7

Figure 7 represents a unity gain follower using an OPAMP. It has actually infinite input resistance and zero output resistance. So the amplifier can be used as a buffer or isolation amplifier.

① It allows the input voltage to be transferred to the output without any change.


② It can be used as an impedance matching device between a high impedance source and a low impedance load.


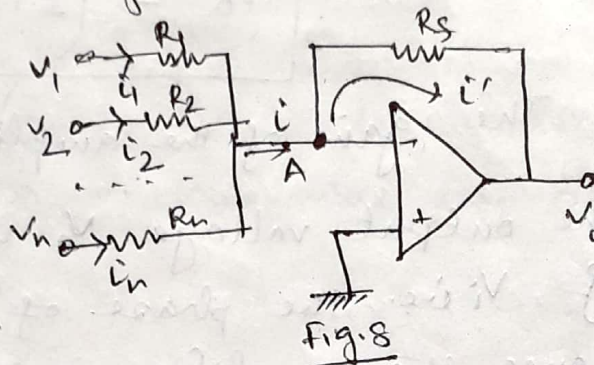
# ADDER OR SUMMING AMPLIFIER

An OPAMP can be used as an adder or summing amplifier. The necessary circuit arrangement is shown in figure 8.

This amplifier basically adds algebraically a number of voltages, each multiplier by a constant gain factor.



Let, the input voltages  $V_1, V_2, \dots, V_n$  are connected to the inverting input terminal of an OPAMP through the resistances  $R_1, R_2, \dots, R_n$ . Let the current passes through these resistances are  $i_1, i_2, \dots, i_n$ . Then the total current flowing through the point A is given by

$$i = i_1 + i_2 + \dots + i_n \quad \text{--- (1) ---}$$

Since, the point A is virtually grounded, the potential of A is zero.

$$\therefore i_1 = \frac{V_1 - 0}{R_1} = \frac{V_1}{R_1}, \text{ Similarly } i_2 = \frac{V_2}{R_2}, \dots, i_n = \frac{V_n}{R_n}$$

$$\therefore \text{From eqn (1), } i = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \quad \text{--- (2) ---}$$

Let  $i'$  current flows through the feedback resistance  $R_f$ . Applying KCL at A, we have,  $i = i'$

$$\text{Now, } i' = \frac{0 - V_0}{R_f} = -\frac{V_0}{R_f} \quad \text{--- (3) ---}$$

$$\therefore -\frac{V_0}{R_f} = \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$

$$\Rightarrow V_0 = -\frac{R_f}{R} \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$

Now, if  $R_1 = R_2 = \dots = R_n = R$  then,

$$V_0 = -\frac{R_f}{R} (V_1 + V_2 + \dots + V_n)$$

$$V_0 = -\frac{R_f}{R} \sum V_n \quad \text{--- (4) ---}$$



Therefore, the output voltage is proportional to the algebraic sum of the input voltages.

② If  $R_f = R$  then,

$$V_o = V_1 + V_2 + \dots + V_n$$

In this case, the output voltage is exactly equal to the sum of the input voltages with a negative sign which may be inverted using another inverting amplifier with unity gain.

③ Choosing  $\frac{R_f}{R_i} = \frac{1}{n}$ , we may obtain the average of  $n$  - input voltages.

## DIFFERENTIAL AMPLIFIER

The circuit diagram of a differential (or difference) amplifier using OPAMP is shown in Fig. 9, whose function is to amplify the difference between two input signals  $V_1$  and  $V_2$ . Since the open loop gain and input impedance of the OPAMP are infinite there exists a virtual short circuit at the input terminals of the OPAMP.

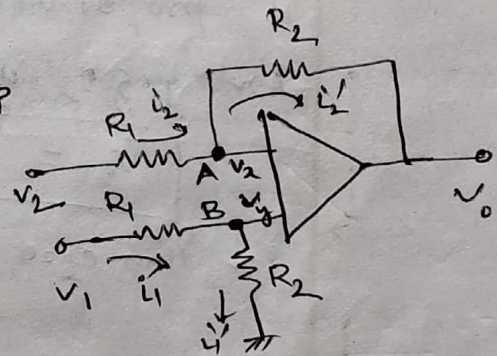


Fig. 9

Let,  $V_x$  and  $V_y$  are the potential at the points A and B respectively and are equal. Also almost same current will flow through  $R_1$  and  $R_2$ .

Let,  $i_1$  and  $i_1'$  currents flow through  $R_1$  and  $R_2$  which are connected to the non-inverting terminal. Then,

According to KCL,  $i_1 = i_1'$

$$\Rightarrow \frac{V_1 - V_y}{R_1} = \frac{V_y - 0}{R_2} \quad \text{--- (1)}$$

Again, let  $i_2$  and  $i_2'$  currents flow through  $R_1$  and  $R_2$  connected at the inverting terminal. Then,  $i_2 = i_2'$

$$\Rightarrow \frac{V_2 - V_x}{R_1} = \frac{V_x - V_o}{R_2} \quad \text{--- (2)}$$



Subtracting equ (2) from eq (1) we have

$$\frac{V_1 - V_2 - V_2 + V_2}{R_1} = \frac{V_2 - V_2 + V_0}{R_2}$$

$$\Rightarrow \frac{V_1 - V_2}{R_1} = \frac{V_0}{R_2} \quad [\text{since, } V_2 = V_2]$$

$$\Rightarrow \boxed{V_0 = \frac{R_2}{R_1} (V_1 - V_2)} \longrightarrow (3)$$

Thus the ckt amplifies the difference of two input voltages.

### Subtractor

A Subtractor produces an output voltage which is proportional to the difference of two input voltages.

In fig 9, if  $R_1 = R_2$ , then eq (3) reduces to,

$$\boxed{V_0 = V_1 - V_2} \longrightarrow (4)$$

In this case, OPAMP acts as a subtractor.

### INTEGRATOR

An OPAMP can be used to implement an integrator whose output voltage is proportional to the integral of the input voltage.

The basic ckt diagram of an integrator is depicted in fig 10. It

is nothing but an inverting amplifier where the feedback resistance is replaced by a capacitor C. Let the input voltage  $V_i$  is applied to the inverting terminal

of the amplifier through a resistance R. Since the input impedance and gain of the OPAMP is infinite, the point A will act as virtual ground.

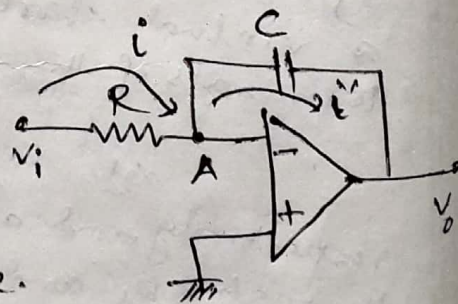


Fig. 10



Let  $i$  and  $i'$  currents flow through  $R$  and  $C$  respectively.  
Applying KCL, at  $A$ , we have  $i = i'$ .

$$\text{Now } i = \frac{V_i - 0}{R_i} = \frac{V_i}{R_i} \quad \text{--- (1)}$$

Also  $i' = \text{current flowing through } C = \frac{dq}{dt}$   
 $dq = \text{charge accumulated on the capacitor in time } dt$

Also,  $q = C(V_i - V_o)$   $C = \text{capacitance}$   
 $= -CV_o$   $V_o = \text{P.D. across the capacitor} = \text{output voltage}$

$$\therefore i' = \frac{dq}{dt} = -C \frac{dV_o}{dt} = \frac{V_i}{R_i} \Rightarrow dV_o = -\frac{1}{CR} (V_i dt) \quad \text{--- (2)}$$

$$\Rightarrow V_o = -\frac{1}{CR} \int V_i dt + K \quad \text{--- (2)}$$

Where  $K = \text{integration constant whose value depends on the initial condition i.e. the initial capacitor voltage.}$

~~At  $t=0$ , the capacitor voltage  $V_i \neq 0$~~

The ~~circuit~~ thus provides an output voltage which is proportional to the ~~rate~~ time integral of the input voltage.

For example, if the input voltage is a sine wave, the output will be a cosine wave; if the input voltage is a square wave, the output will be a triangular wave.

## DISCUSSIONS

The basic integrator ~~circuit~~ of fig 10 has the problem of d.c. stability. Since the capacitor is open to d.c. signals, the d.c. gain of the amplifier is infinite, because,  
the capacitive reactance  $X_c = \frac{1}{j\omega C} = \frac{1}{0} = \infty$   
and thus gain  $= A = \frac{X_c}{R} = \infty$ .

As a result, any offset voltage may ~~drive~~ drive the opamp output to a saturation.

A way out of this difficulty is to decrease the d.c. gain by inserting a resistance  $(R_i)$  parallel with  $C$  as shown in fig. 11. The value of  $R_i$  is so chosen that the time constant  $CR_i$  becomes large compared to



to period of the input voltage.

Also to minimise ~~Page No.~~ 18 the error due to offset a resistance  $R_2$  (~~ANSWER SHEET~~)  $= R_1 || R_1$  may be added between the non-inverting terminal and the ground.

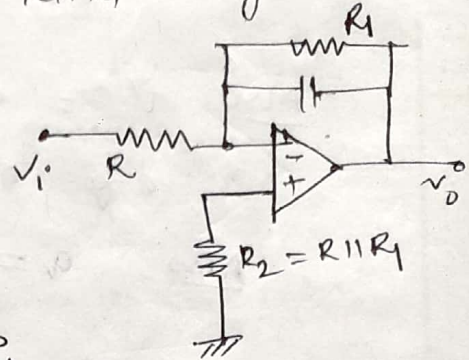


Fig 11

### Applications:

The integrator ckt are widely used in digital voltmeters, in sweep or ramp (i.e. voltage varying linearly with time) generators and simulation studies in analog computers.

## DIFFERENTIATOR

A differentiator provides an output voltage proportional to the time derivative of the input voltage. The basic ckt. diagram of a differentiator using an OPAMP is shown in fig. 12. Here, the differentiator ckt is nothing but an inverting amplifier where the input resistance is replaced by a capacitor  $C$ .

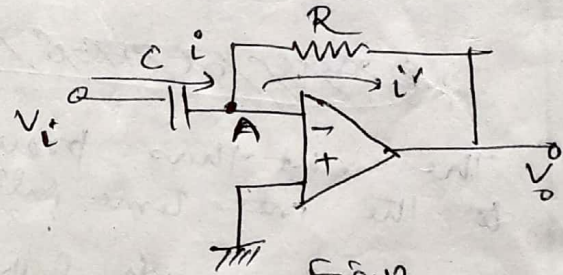


Fig 12

Since the input impedance and gain of an ideal OPAMP is infinite, the point A will act as a virtual ground.

Let  $i$  and  $i'$  are currents flow through the capacitor and the feedback resistance  $R$ .  $V_i$  and  $V_o$  are the input and output voltages.

Now, according to KCL at A,  $i = i'$ .

Here  $i = \frac{dq}{dt}$  with  $q = eV_i$ .

$$\therefore i = C \frac{dV_i}{dt} \quad \text{--- (1)}$$

$$\text{also, } i' = 0 - \frac{V_o}{R} = -\frac{V_o}{R} \quad \text{--- (2)}$$

From (1) and (2)  $-\frac{V_o}{R} = C \frac{dV_i}{dt} \Rightarrow \boxed{V_o = -CR \frac{dV_i}{dt}} \quad \text{--- (3)}$



Thus, from eq (3), it is clear that the output voltage of the ckt is proportional to the time derivative of the input voltage. The constant of proportionality (ex. scale factor) being  $-CR$ .

(ANSWER SHEET)  
 For example, if the input voltage is a sine wave the output will be a ~~be~~ cosine wave and if the input is a square wave the output will be a triangular wave.

## DISCUSSIONS

If the input signal is  $V_i = V_0 \sin \omega t$  then the output voltage will be,  $V_0 = -V_0 \omega CR \cos \omega t \rightarrow (4)$

∴ the output voltage  $V_0 \propto \omega$   
 that means that the differentiator behaves as a simple frequency-to-voltage converter, and the magnitude of the output voltage changes linearly with the frequency of the input voltage.

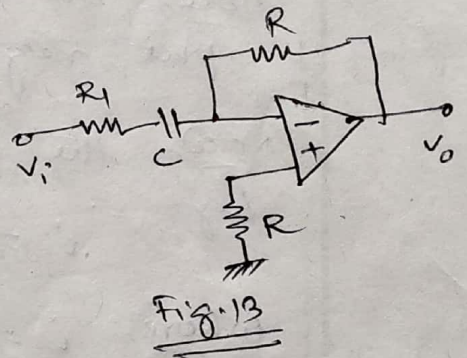


Fig. 13

The ckt has high gain at high frequencies and thus it amplifies high frequency noise and switching spikes. The ckt is found to be very much unstable. To avoid this difficulty, a resistor  $R_1$  having magnitude  $\frac{R}{10}$  to  $\frac{R}{100}$  is connected in series with  $C$ . The resistor  $R_1$  limits the high frequency gain and makes the practical differentiator useful only for frequency ~~at~~ well below the limiting frequency given by  $1/2\pi CR_1$ .

## Applications:

The differentiator is used in wave-shaping ckt to detect high frequency components. It is also used as a rate-of-change detector in FM modulators.



# LOGARITHMIC AMPLIFIER

If the feedback resistor of an inverting amplifier is replaced by a p-n junction diode, we obtained a logarithmic amplifier which gives an output voltage proportional to the logarithmic of the input voltage. The ckt. of a logarithmic amplifier is shown in fig. 13.

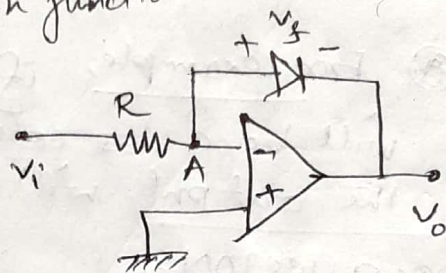


Fig 13.

Here, the input voltage is  $V_i$ , input resistance is  $R$  and the output voltage is  $V_o$ .

Now, the volt-ampere characteristics of a diode is given by,

$$i = I_s \left( e^{\frac{eV_f}{\eta kT}} - 1 \right) \quad \text{--- (1)}$$

where,  $i$  = instantaneous current passing through the diode for forward voltage  $V_f$ .

$I_s$  = reverse saturation current

$k$  = Boltzmann constant =  $1.3807 \times 10^{-23}$  J/K

$T$  = Absolute temp. of the diode

$\eta$  = constant = 1 for Ge diodes and 2 for Si diodes

If  $e^{eV_f/\eta kT} \gg 1$  then,

$$i \approx I_s e^{eV_f/\eta kT} \Rightarrow \frac{i}{I_s} = e^{eV_f/\eta kT}$$

$$\Rightarrow \ln\left(\frac{i}{I_s}\right) = \frac{eV_f}{\eta kT} \Rightarrow V_f = \frac{\eta kT}{e} \ln\left(\frac{i}{I_s}\right) \quad \text{--- (2)}$$

Since, the input impedance and gain of the OPAMP is infinite hence, the point A is a virtual ground.

hence,  $i = \frac{V_i - 0}{R} = \frac{V_i}{R} \quad \text{--- (3)}$

Thus from eq (2)  $V_f = \frac{\eta kT}{e} \ln\left(\frac{i}{I_s}\right)$

$$\therefore V_o = - \frac{\eta kT}{e} \ln\left(\frac{V_i}{I_s R}\right) = -V_o$$

So,  $V_o$  is proportional to the logarithm of input voltage  $V_i$ .



# FREQUENCY RESPONSE OF OPAMP

Fig. 14 represents the ~~open loop~~ small-signal frequency response characteristics of a typical IC OPAMP. The OPAMP can show gain instability. For this internal compensating capacitors are used which make the open loop bandwidth or upper cut off frequency  $f_{L}(OL)$  or the frequency at which the gain drops to  $\frac{1}{2}$  of the d.c. gain, very low. For IC OPAMP 741 the cut off frequency  $f_{L}(OL)$  is of the order of 10 Hz. For this an open loop OPAMP is not suitable for linear applications.

For an ideal OPAMP the bandwidth is infinity, but for practical OPAMP the open loop gain is only 10 Hz. Thus the frequency response of the OPAMP is considered under closed loop condition.

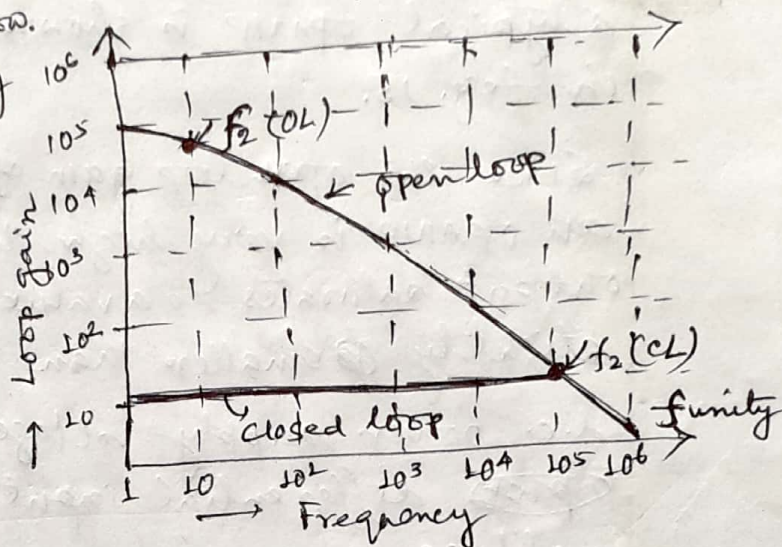


Fig. 14

## SLEW RATE:

The maximum rate at which OPAMP's output can change is called the slew rate. It is usually expressed in V/ $\mu$ s. For IC 741 OPAMP, the slew rate is about 0.5 V/ $\mu$ s.

① The speed limit on ~~output~~ how fast the output of the OPAMP can change arises due to the fact that the internal compensating capacitor must be charged or discharged before the output voltage can change to different levels.

② If one tries to ~~change~~ drive the output at a rate of voltage change greater than the slew rate the output becomes distorted.



# INPUT- OUTPUT CHARACTERISTICS OF OPAMP

The basic nature of the input-output open-loop characteristics of a typical opamp is shown in fig. 15.

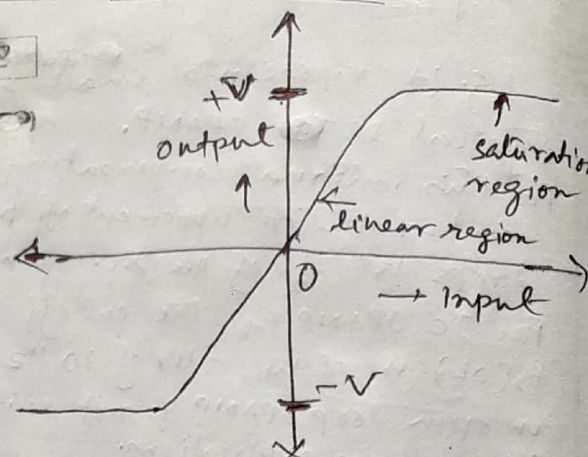


Fig. 15

Since the open loop gain of an opamp is very high, the output saturates to a value slightly smaller than the d.c. power supply voltage ( $\pm V$ ) as the magnitude of the ~~input~~ differential input voltage exceeds only a very small voltage.

For the saturation region, the output of the opamp does not change with the input but remains constant at the supply voltages.

For IC 741 opamp, this voltage is usually  $\pm 15V$  or  $\pm 12V$ . Thus the linear region of operation is limited to a small region around the origin.

For practical opamp the curve may not pass through the origin due to the presence of offset voltage.

However, the minimum input voltage  $V_{min}$  that causes saturation is given by,  $V_{min} = \pm \frac{V_{sat}}{A}$ , where  $A$  is the open loop gain.

For example, If  $\pm V_{sat} = \pm 12V$  and  $A = 10^5$  then


$$V_{min} = \pm \frac{12}{10^5} = \pm 0.12 mV$$

This means that that the input voltage more positive than  $+0.12V$  will give positive saturation and input voltage more than  $-0.12V$  will drive negative saturation voltage. So linear operation the input of opamp should be restricted to very small values. This makes an open loop opamp unsuitable for linear operation.


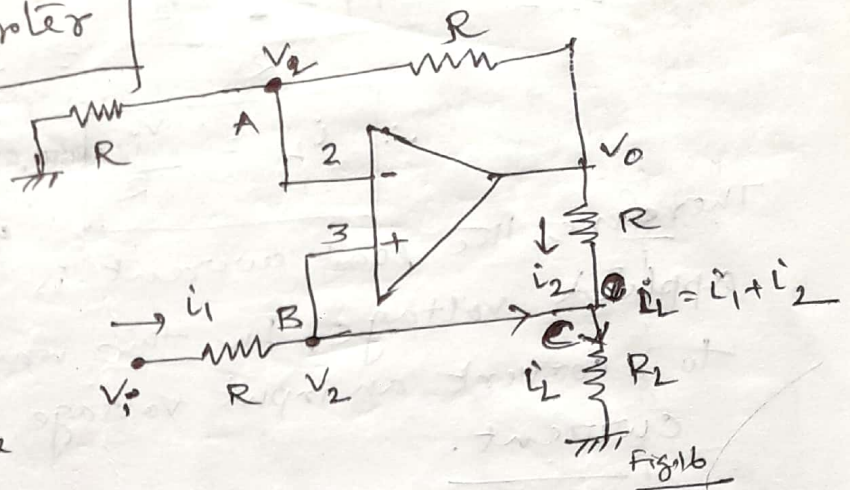
# Voltage to current Converter

Very often it becomes necessary to convert a voltage signal to a proportional output current. An OPAMP can be successfully applied in this purpose. A voltage



to current converter using an OPAMP is shown in the figure. The input voltage is usually applied to the inverting terminal of an OPAMP. The input voltage  $V_1$  is applied to the non inverting terminal through a resistance  $R$ , whereas the inverting input terminal is grounded through another resistance  $R$ . The feedback resistance is also taken as  $R$ . The output terminal is connected to  $R_L$  through  $R$ , where  $R_L$  (load resistance) is grounded. Let the potentials at the point A and B are  $V_1$  and  $V_2$  respectively. The input current is  $i_1$ , output current is  $i_2$  and the load current is  $i_L$ .

Then, according to KCL at C,  $i_L = i_1 + i_2 \longrightarrow \textcircled{1}$

$$\text{Now, } i_1 = \frac{V_1 - V_2}{R} \quad \text{and} \quad i_2 = \frac{V_0 - V_2}{R} \quad [V_0 = \text{output voltage}]$$

$$\therefore i_L = \frac{V_1 - V_2}{R} + \frac{V_0 - V_2}{R}$$

$$i_L = \frac{V_1 + V_0 - 2V_2}{R} \longrightarrow \textcircled{2}$$

Since the input voltage is applied to the non-inverting amplifier, the gain of the amplifier is  $= \left(1 + \frac{R}{R}\right) = 2$

Further, the effective voltage treated as the input voltage is  $= V_2$

$$\therefore \text{Gain} = \frac{V_0}{V_2} = 2 \Rightarrow V_0 = 2V_2$$

Substituting the value of  $V_0$  in eq  $\textcircled{2}$  we have,



$$I_L = \frac{V_1 + 2V_2 - 2V_2}{R} = \frac{V_1}{R}$$

$$\therefore \boxed{I_L = \frac{V_1}{R}} \quad \text{ie. } (I_L \propto V_1 \text{ when } R = \text{const.})$$

Therefore, the load current is directly proportional to the applied voltage. In this way an OPAMP can be employed to convert an input voltage to its proportional output current.

## Current to voltage converter

Very often we need to convert a current to its proportional voltage. In this purpose OPAMP is used widely. For example as we know that the output voltage of a sensor can not be sent to a large distance due to creation of noise. In that case, that voltage is first converted into current and send it to a distant place. Then using a current to voltage converter we can easily convert the current into voltage.

The ckt. diagram of a current to voltage converter using an OPAMP is shown in the figure. The current source is connected directly to the inverting input terminal and the non-inverting terminal is grounded. The feedback resistance used is  $R$ .

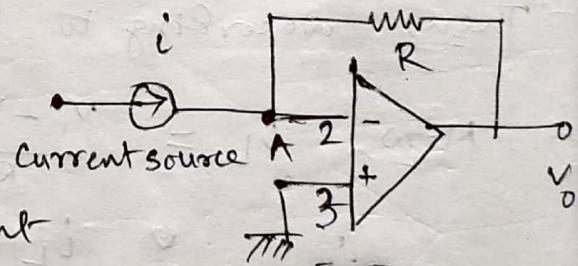


Fig-17

According to the concept of virtual ground, the point A will act as virtual ground. As a result, the input current  $i$  will flow through  $R$ .

The ~~voltage~~ output voltage  $V_o$  = voltage across the feedback resistance

$$\Rightarrow V_o = -Ri \quad [\text{-ve sign arises due to application of input current to the inverting terminal}]$$





$$V_o \propto i$$

Obviously, the output voltage is proportional to the input current.
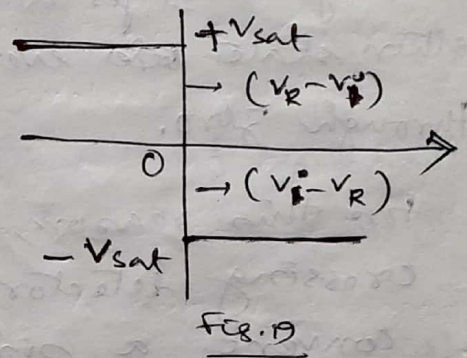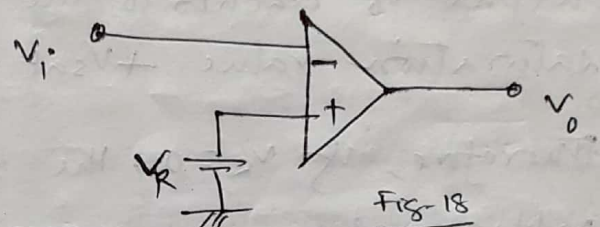
## Voltage Comparator

compare two voltages, the comparator ckt. is used. The figure shown side represents a comparator using OPAMP to compare an input voltage  $V_i$  (given to the inverting terminal of the OPAMP) with a reference voltage  $V_R$  (given to the non-inverting terminal of the OPAMP).




As long as  $V_i < V_R$  the output voltage  $V_o$  goes to a maximum positive <sup>saturation</sup> voltage  $+V_{sat}$  (say). As the input voltage crosses  $V_R$  and goes towards the region  $V_i > V_R$ , the output voltage switches to the negative saturation voltage  $-V_{sat}$  (say). Therefore, looking at the output voltage profile, one can easily identify whether the voltage  $V_i$  is greater than or less than  $V_R$ .

The comparator can be used to generate a systematic square wave from a sine wave, by just taking  $V_R = 0$  and choosing  $V_i$  as a sinusoidal voltage.



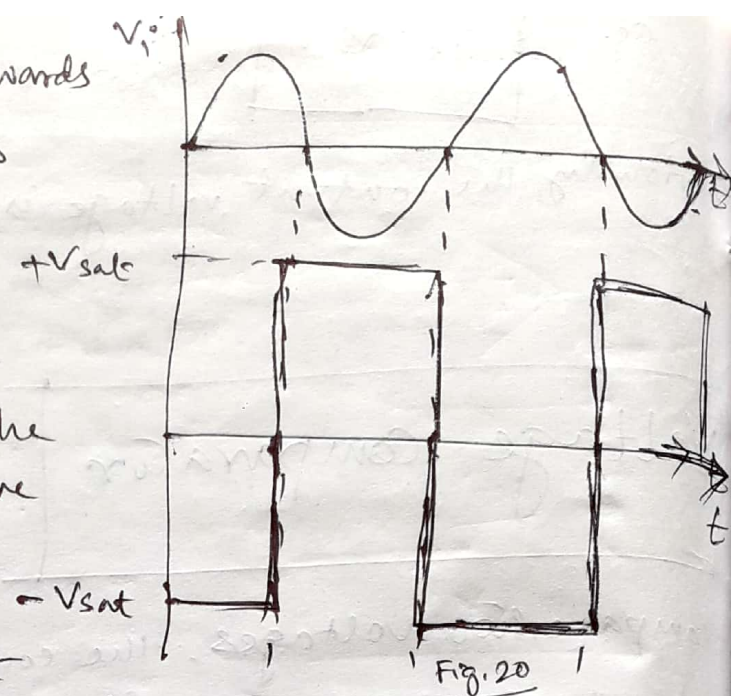When  $V_i$  passes through zero towards positive values, the output  $V_o$  is driven into negative saturation voltage  $-V_{sat}$ . On the other hand, when  $V_i$  passes through zero towards negative values, the output  $V_o$  reaches to the positive saturation value  $+V_{sat}$ .




Therefore, if  $V_R = 0$ , the output voltage changes almost discontinuously from one state to the other state ~~the~~ every time when the input voltage passes through zero.

For this reason, such a configuration is called a zero-crossing detector. This type of ckt. is often used to convert a sinusoidal waveform into square waveform.
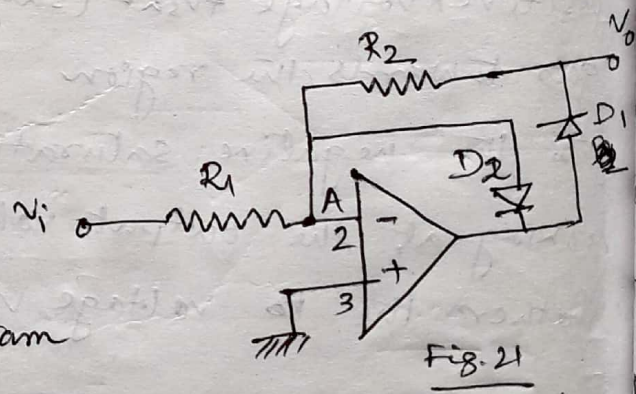
## Half-wave rectifier


An OPAMP can be used as half-wave rectifier. The ckt diagram

of a half-wave rectifier using an OPAMP is shown in the figure. Here, the sinusoidal input voltage  $V_i$  is given to the inverting ~~and~~ input-terminal through the resistance  $R_1$ . The non-inverting terminal is grounded. The feedback resistance  $R_2$  is used in this ckt. diagram. The diodes  $D_1$  and  $D_2$  are connected as shown in the figure.





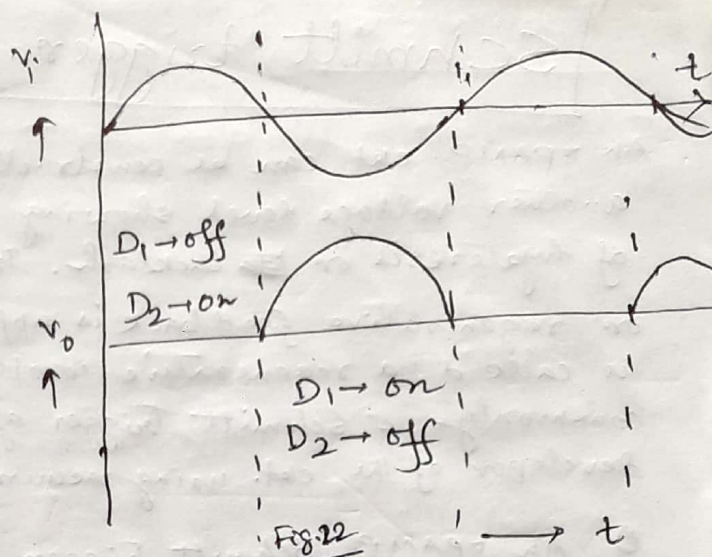The output voltage profile of a half-wave rectifier is shown in the figure beside. For the positive half-cycle of the applied input ac voltage, the <sup>diode</sup>  $D_2$  become active and the diode  $D_1$  is off, since  $D_2$  then becomes forward biased so current will pass through the diode  $D_2$ .



Neglecting the diode resistance, the output ~~v\_o~~  $v_o$  will be zero, because  $v_o = -\frac{\text{diode resistance } v_i}{R_1}$ . i.e.  $v_o = 0$ . However, in this case the diode is virtually grounded to the point A (since the diode resistance is neglected). Therefore, the output voltage in the positive half cycle will be zero (as shown in the fig.).

Now, during the negative half-cycle of the input voltage, the  $D_1$  will be forward biased and hence will active (on), on other hand the diode  $D_2$  will be reversed biased and thus current will pass through  $D_2$ . Neglecting the diode

resistance, the gain of the amplifier will be  $-\frac{R_2}{R_1}$ . Thus the output voltage is  $v_o = -\frac{R_2}{R_1} v_i = \frac{R_2}{R_1} v_i$ . Therefore, output voltage will be found for the negative half-cycle. In



this way, OP-AMP can be used as a half-wave rectifier.


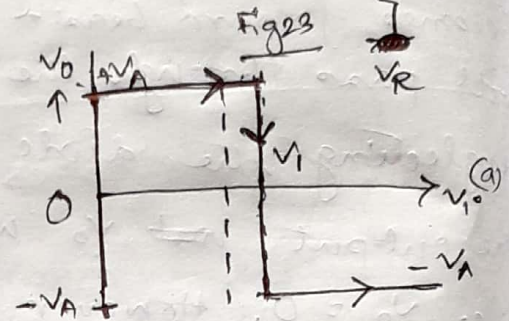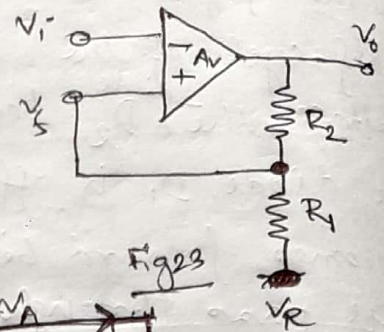
# Schmitt trigger or regenerative comparator

An OPAMP ckt can be constructed to switch from one voltage level to another voltage level showing the phenomenon of hysteresis or ~~the~~ backlash. In this case positive or regenerative feedback is applied. Such a ckt. is called a regenerative comparator or more commonly a Schmitt trigger after the original developer of the ckt. using vacuum tubes.

● An OPAMP Schmitt trigger is shown in fig 23. The input voltage  $V_i$  is applied to the inverting terminal and the feedback voltage  $V_f$  is applied to the non-inverting terminal.



● From the superposition theorem we get,

$$V_f = \frac{R_1 V_o}{R_1 + R_2} + \frac{R_2 V_R}{R_1 + R_2} \quad \text{--- (1)}$$


If,  $V_i$  is small or negative such that  $V_i < V_f$ , then the output of the amplifier will saturates to  $V_o = +V_A$ , where  $+V_A$  is the +ve saturation voltage.

therefore, 
$$V_f = \frac{R_1 V_A}{R_1 + R_2} + \frac{R_2 V_R}{R_1 + R_2} = V_1 \text{ (say)} \quad \text{--- (2)}$$

Let now,  $V_i$  increase in the +ve direction.

The value of  $V_o$  will remain unchanged to  $+V_A$  till  $V_i$  attains the threshold, critical or trigger voltage  $V_1$ .

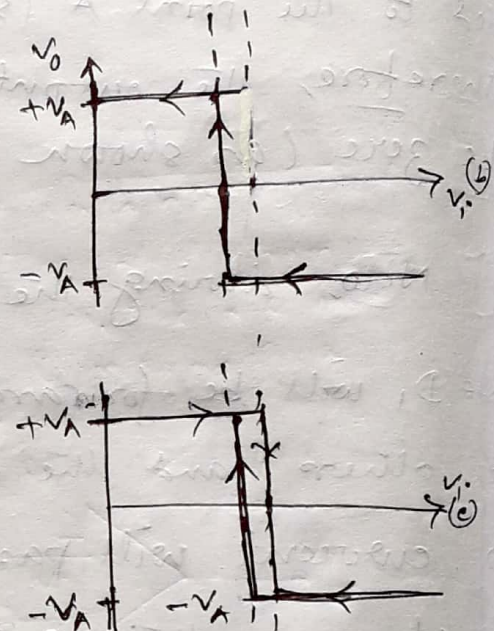At this trigger voltage, the output of the amplifier switches to  $V_o = -V_A$ , because in this case  $V_i$  just exceeds  $V_1$  and thus  $V_o$  and  $V_f$  will decrease. Thus  $(V_i - V_f)$  increases to decrease  $V_o$  further. This cumulative action takes place rapidly to bring  $V_o$  immediately to  $-V_A$ . The output voltage  $V_o$  is sticks to  $-V_A$  as long as  $V_i > V_1$ .



For  $V_i > V_1$  we have,

$$V_f = \frac{R_2 V_R}{R_1 + R_2} - \frac{V_A R_1}{R_1 + R_2} = V_2 \text{ (say)} \quad \text{--- (3)}$$



The switching action occurs only if the amplification is sufficiently large so that small changes in  $V_i$  are amplified to the desired extent. The feedback factor is  $\beta = \frac{R_1}{R_1 + R_2}$ . The ckt. will function satisfactorily provided the loop gain  $-\beta A_v$  is much larger than unity.

Suppose that we now decrease  $V_i$ . Then the output will remain at  $-V_A$  till  $V_i = V_2$ . A regenerative transition will occur at this point as shown in fig 24(b), so that  $V_o$  will switch to  $+V_A$  instantaneously.

The overall transfer characteristics of the Schmitt trigger is shown in fig 24(c). This curve will be called a hysteresis curve because it has the form of a magnetic hysteresis loop.

The hysteresis curve shows that the ckt triggers at a higher voltage for increasing input signals than for decreasing input signals.

The width of the hysteresis loop is given by,

$$V_H = V_1 - V_2 = \frac{2R_1 V_A}{R_1 + R_2} \quad \text{--- (4)}$$

In order to reduce  $V_H$ , we have to make  $\frac{R_1}{R_1 + R_2}$  small. But it can not be reduced greatly, for otherwise the loop gain  $-\beta A_v$  becomes small.

### Example

Suppose we have to design a Schmitt trigger for which  $V_R = 3V$ , and  $V_H = 0.03V$ , using an OPAMP for which  $V_A = 5V$  and  $A_v = -20000$ . Then,

$$V_H = \frac{2R_1 V_A}{R_1 + R_2} = \frac{5 \times 2 R_1}{R_1 + R_2} = 0.03$$

$$\Rightarrow \frac{R_1}{R_1 + R_2} = 0.003 = \beta$$

$$\text{The loop gain is } \cancel{A_v \beta} = \frac{A_v R_1}{R_1 + R_2} \quad \underline{\underline{(-\beta A_v)}}$$

$$= -20000 \times 0.003 = -60$$

This is much larger than 1, and is therefore acceptable.



## Applications

● An important application of the Schmitt trigger is to transform a slowly varying input voltage into a square voltage at the output.

● The Schmitt trigger is a comparator because the ckt. compares an input voltage with the trigger levels  $V_1$  and  $V_2$  for the output voltage to swing between  $-V_A$  and  $+V_A$ . It is a regenerative comparator because it employs positive or regenerative feedback.

## WIEN BRIDGE OSCILLATOR

Wienbridge oscillator is an RC oscillator which is widely used in the laboratory as an AF signal generator. The ckt. diagram of a Wienbridge oscillator using OPAMP is depicted in fig. 25. The R-C combination and the resistors  $R_1$  and  $R_2$  form the four arms of a Wien bridge. The simplified ckt. of fig. 25 is shown in fig. 26. The output  $v_i$  of the bridge (betw. points A and B of fig. 26) is amplified by the OPAMP, which has very large positive voltage gain, very high input impedance and negligible output impedance. The output  $v_o$  of the amplifier becomes the input of the bridge supply voltage.

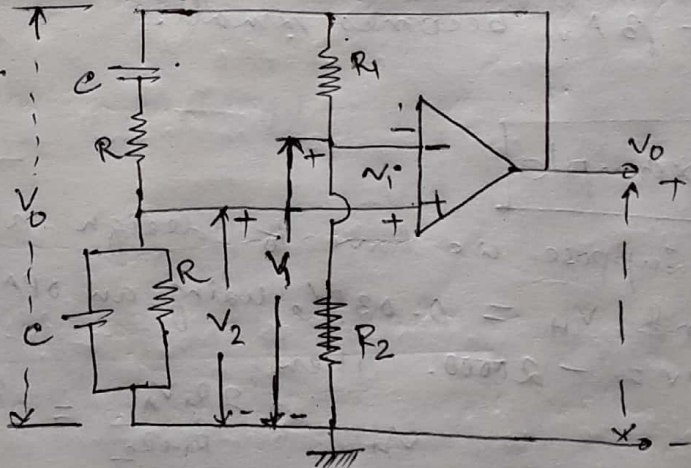


Fig. 25: Ckt. diagram of Wien bridge oscillator using OPAMP.

The oscillator operates with the bridge slightly unbalanced and sufficient amplification to establish a loop gain of unity. The ckt. uses positive feedback through RC combinations to the non-inverting input terminal of the OPAMP. As the non-inverting ~~terminal~~ of OPAMP introduces no phase shift, the feedback



voltage  $V_2$  must be in phase with  $V_0$  to satisfy Barkhausen criterion for oscillation.

When the bridge is balanced, we have

$$\frac{R_1}{R_2} = \frac{R + \frac{1}{j\omega C}}{R \parallel j\omega C} \rightarrow (1)$$

$$\text{Now, } R \parallel j\omega C = \frac{1}{\frac{1}{R} + j\omega C}$$

$$= \frac{R}{1 + j\omega CR}$$

$$\therefore \frac{R_1}{R_2} = \frac{R(1 + \frac{1}{j\omega CR})}{R \frac{1}{1 + j\omega CR}}$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{(1 + j\omega CR)}{j\omega CR} \times (1 + j\omega CR) = \frac{(1 + j\omega CR)^2}{j\omega CR}$$

$$\frac{R_1}{R_2} = \frac{1 + 2j\omega CR - \omega^2 CR^2}{j\omega CR} = 2 + \frac{1 - \omega^2 CR^2}{j\omega CR} \rightarrow (2)$$

Equating the real and imaginary parts on the both sides of eq (2), we have

$$\frac{R_1}{R_2} = 2 \Rightarrow R_1 = 2R_2 \rightarrow (3)$$

and,  $\frac{1 - \omega^2 CR^2}{j\omega CR} = 0 \Rightarrow \omega^2 CR^2 = 1$

$$\Rightarrow R = \frac{1}{\omega C} \text{ with } \omega = \frac{1}{CR}$$

$\therefore$  the frequency of oscillation  $\omega$

$$f = \frac{\omega}{2\pi} = \frac{1}{2\pi RC} \rightarrow (4)$$

When the bridge is balanced, then the voltage across the two lower arms (between A and B) must be equal, i.e.

$$V_1 = V_2 = \frac{R_2}{R_1 + R_2} V_0 = \frac{R_2}{3R_2} V_0 = \frac{1}{3} V_0 \quad [\text{from eq (3)}]$$

Therefore, at balanced condition, we get,  $\frac{R_2}{R_1 + R_2} = \frac{1}{3} \rightarrow (5)$

and,  $\frac{V_1}{V_0} = \frac{V_2}{V_0} = \frac{1}{3} \rightarrow (6)$

Since,  $V_1 \neq 0$  which nothing but  $(V_1 - V_2)$  for oscillation to occur, the ratio  $R_2/(R_1 + R_2)$  is taken to be less than  $1/3$ . If we let,

$$\frac{R_2}{R_1 + R_2} = \frac{1}{3} - \delta \rightarrow (7) \quad \text{where, } \delta \text{ is a number greater than } 0, \text{ then the bridge is}$$

slightly unbalanced and gives a feedback voltage  $V_f$ .

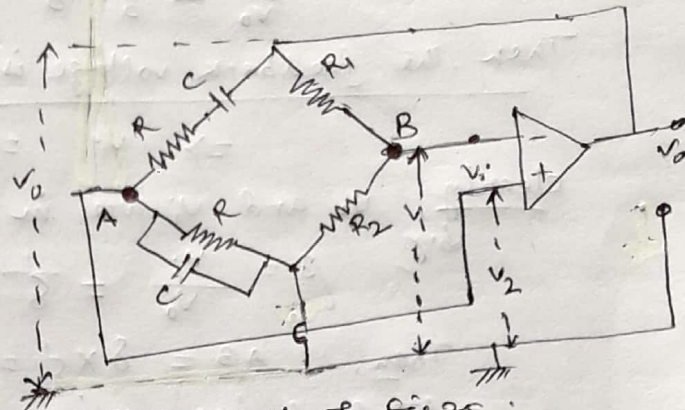


Fig 28: Equivalent circuit of Fig 25.



As the bridge is unbalanced by adjusting the ratio  $\frac{R_1}{R_2}$ , the ratio  $V_1/V_0$  remains  $1/3$  but  $V_2/V_0$  ratio changes which is given by,

$$\frac{V_2}{V_0} = \frac{1}{3} - \delta$$

Then the feedback voltage is given by,  $V_i = V_1 - V_2 = \left(\frac{1}{3} - \frac{1}{3} + \delta\right) V_0$

$$\Rightarrow V_i = \frac{V_0}{\delta}$$

clearly,  $V_0$  and  $V_i$  are in phase, and the feedback fraction is given by,

$$\beta = \frac{V_i}{V_0} = \frac{1}{\delta} \quad \text{Further the gain } A = \frac{V_0}{V_i} = \delta = \frac{1}{\beta}$$

Then,  $A\beta = \delta \times \frac{1}{\delta} = 1$  i.e. the Barkhausen criterion is satisfied by making  $\delta > 3$ .

Application: Like wise phase-shift oscillator, Wienbridge oscillator is used in the AF range. Continuous variation of frequency is achieved by varying the <sup>two</sup> capacitors. This is an advantage over phase-shift oscillator, where three capacitors are varied simultaneously.

The Wien-bridge oscillator has the following advantages:

- (i) The overall gain is very high since high <sup>gained</sup> amplification network (OPAMP) is used.
- (ii) The circ. gives a very good sine wave output.
- (iii) The frequency stability is very good. The frequency of oscillation remains markedly constant over a fairly long time interval.
- (iv) The frequency of oscillation can be easily varied.

Disadvantages: the disadvantages of this oscillator is:

very high frequency can not be generated with Wien bridge oscillator.